

## + Ripple Carry Adder:

A **Ripple Carry Adder (RCA)** is a fundamental digital circuit used to perform binary addition. It consists of multiple full adders connected in series, where each full adder is responsible for adding corresponding bits from two binary numbers along with a carry bit from the previous stage. The carry output from each full adder "ripples" to the next, hence the name.

### + Structure and Operation:

- **Full Adders in Series:** An RCA is constructed by cascading full adders, with the carry output of one feeding into the carry input of the next.
- **Carry Propagation:** The carry signal propagates through each stage, which can introduce a delay proportional to the number of bits being added.

### + Advantages:


- **Simplicity:** The design is straightforward and easy to implement.
- **Scalability:** It can be extended to add numbers of any bit length by increasing the number of full adders.

### + Disadvantages:


- **Propagation Delay:** The main drawback is the cumulative delay caused by each carry bit waiting for the previous one, making it slower for large bit-width additions.
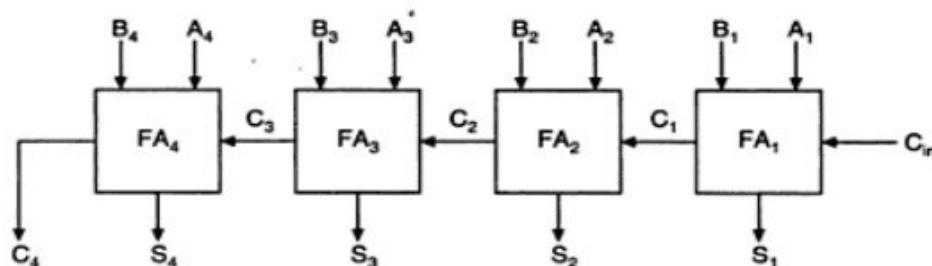
## + 4-bit Ripple Carry Adder

- The below diagram represents the 4-bit ripple-carry adder. In this adder, four full adders are connected in cascade.  $C_0$  is the carry input bit and it is zero always. When this input carry ' $C_0$ ' is applied to the two input sequences  $A_1 A_2 A_3 A_4$  and  $B_1 B_2 B_3 B_4$  then output represented with  $S_1 S_2 S_3 S_4$  and output carry  $C_4$ .



## Simulation Waveforms:

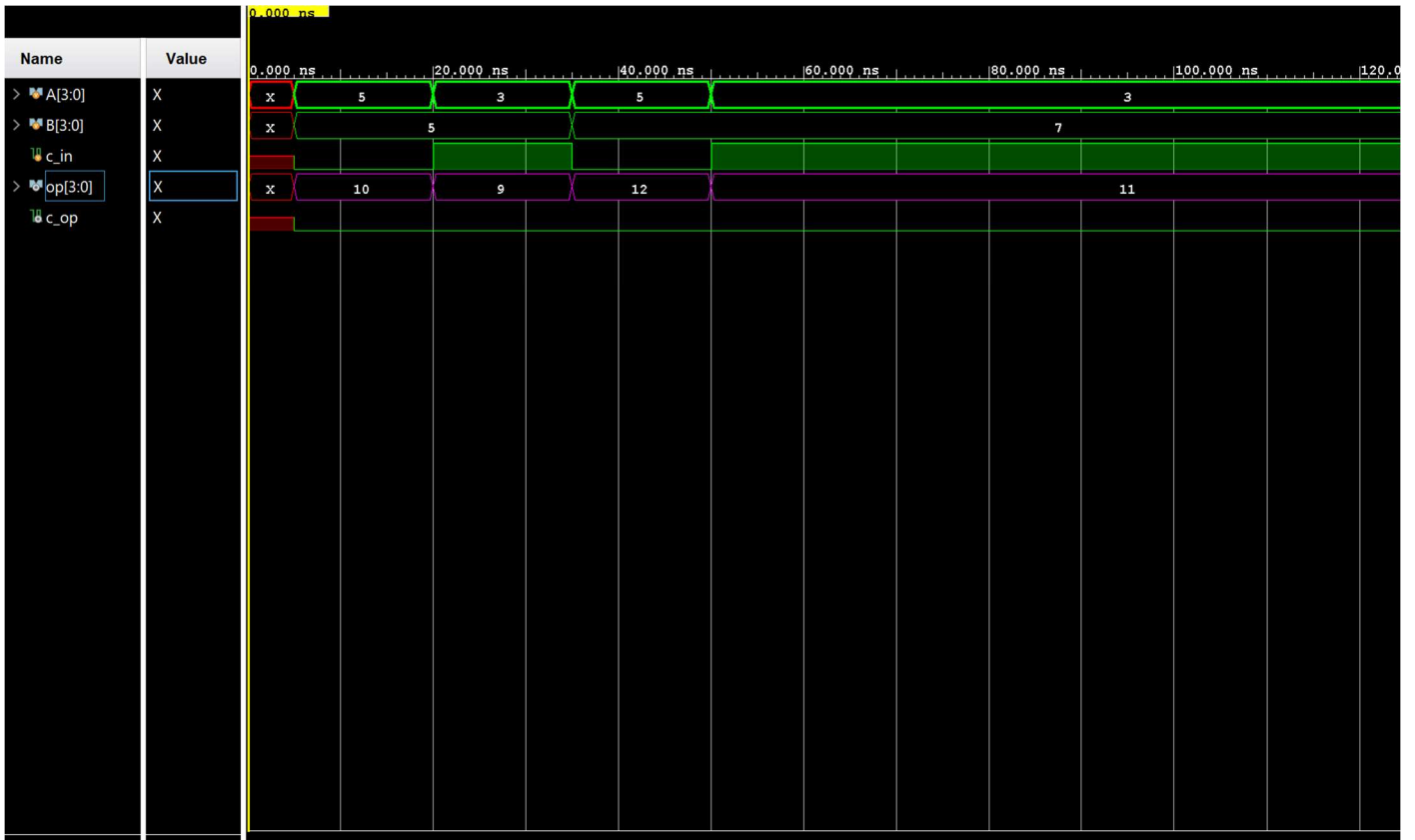

## Schematic:

